

Rafay Aamir

Bsec 19047

Machines - A2

Q1  
a)

$S = 50 \text{ KVA}, 2400-240, 60 \text{ Hz}$


i)  $R_p = 0.72, X_p = j0.92, R_s = 0.007, X_s = j0.009,$   
 $R_c = 6.32, X_m = j43.7, a = \frac{2400}{240} = 10$

$$R_s' = (0.007)(10^2) = 0.7 \Omega$$

$$X_s' = (j0.009)(10^2) = j0.9 \Omega$$

$$R_c' = (6.32)(100) = 632 \Omega, X_m' = (j43.7)(100) = j4370 \Omega$$
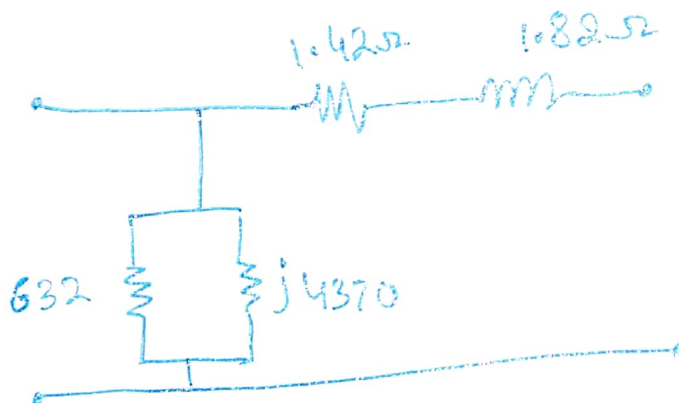
$$R_{eq} = R_p + R_s' = 1.42 \Omega, X_{eq} = X_p + X_s' = 1.82 \Omega$$




ii)

$$R_p' = (0.72)/100 = 0.0072 \Omega$$

$$X_p' = j0.92/100 = j0.0092 \Omega$$

$$R_{eq} = R_s + R_p' = 0.0142 \Omega$$

$$X_{eq} = X_s + X_p' = j0.0182 \Omega$$

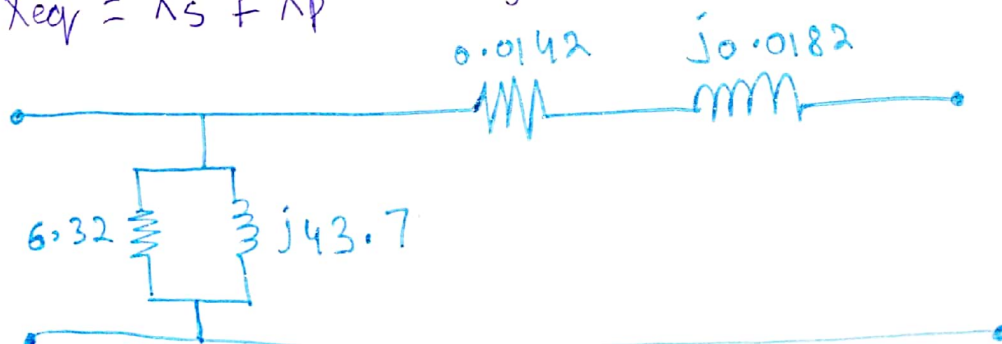

⑥ (i)  $Z_{\phi} = 632 + j4370$  ,  $|Z_{\phi}| = 4415.5 \Omega$

$$I_H = \frac{V_H}{|Z_{\phi}|} = \frac{2400}{4415.5} \quad , \quad \boxed{I_H = 0.54 \text{ A}}$$

⑦ (ii)  $Z_{\phi} = 6.32 + j43.7$  ,  $|Z_{\phi}| = 44.155 \Omega$

$$I_L = \frac{V_L}{|Z_{\phi}|} = \frac{240}{44.155} \quad \boxed{I_L = 5.43 \text{ A}}$$

Q:-2

①  $S = 50 \text{ kVA}$  ,  $V_H = 48 \text{ V}$  ,  $I_H = 20.8 \text{ A}$  ,  $P = 617 \text{ W}$

$$Z_{eq} = \frac{V_H}{I_H} = \frac{48}{20.8} \quad , \quad Z_{eq} = 2.3 \Omega$$

$$R_{eq} = \frac{P}{I_H^2} = \frac{48}{(20.8)^2} \frac{617}{(20.8)^2} = 1.426 \Omega$$

$$X_{eq} = \sqrt{|Z_{eq}|^2 - R_{eq}^2} = \sqrt{2.3^2 - 1.426^2} \Rightarrow 1.804$$

$$P = PF \times S = (0.8)(50 \text{ k}) \quad , \quad \boxed{P = 40 \text{ kW}}$$

$$P_{loss} = I_H^2 \times R_{eq} = (20.8^2)(1.426) \quad , \quad P_{loss} = 616.9 = 617 \text{ W}$$

$$P_{loss} = 617 + 166 \Rightarrow 803 \text{ W}$$

$$P_{in} = 40000 + 803 = 40803 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{40 \text{ k}}{40.803 \text{ k}} \times 100 \quad , \quad \boxed{\eta = 98 \%}$$

$$VR = \frac{2400 - (20.8 \angle -36.8)(1.426 + j1.82) - 2400}{2400 - (20.8 \angle -36.8)(1.426 + j1.82)} \times 100 \quad \boxed{VR = 2 \%}$$

⑤  $PF = 1$  ,  $P = 50 \text{ kW}$  ,  $\theta = 0^\circ$

$$I_H = \frac{P}{V} = \frac{50000}{2400} = 20.83 \text{ A}$$

$$VR = \frac{R \{ 2400 + (20.83)(1.42 + j1.82) \} - 2400}{R \{ 2400 + (20.83)(1.42 + j1.82) \}} \times 100$$

$$VR = 1.2 \%$$

Q:- 3

①  $V_H = V_{ab} + V_{bc} = V_{ab} + V_L \Rightarrow 240 + 2400$

$$V_H = 2640 \text{ V}$$

②  $I_R = \frac{S}{V_R} = \frac{50 \text{ kVA}}{240}$  ,  $I_R = 208.3 \text{ A}$

$$P = V_H I_R = 2640 \times 208.3$$

$$P = 550 \text{ kVA}$$

$$I_L = \frac{2640}{2400} \times 208.3$$

$$I_L = 229 \text{ A}$$

③ from question 2 ,  $P_{\text{loss}} = 803 \text{ W}$

$$P_{\text{in}} = (0.8) \times (55 \times 10^3) + 803$$

$$P_{\text{in}} = 44803 \text{ W}$$

$$P_{\text{out}} = (0.8) (55000) = 44000 \text{ W}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\% = \frac{44000}{44803} \times 100$$

$$\eta = 99.8 \%$$

Q:-4  $S = 50 \text{ KVA}$  ,  $V_H = 2400 \text{ V}$  ,  $V_L = 240 \text{ V}$

$$I_H = \frac{S}{V_H} = \frac{50 \text{ KVA}}{2400} , I_H = 20.83 \text{ A}$$

$$I_L = \frac{S}{V_L} = \frac{50 \text{ KVA}}{240} , I_L = 208.3 \text{ A}$$

$$\frac{V_H}{V_L} = \frac{2400}{240} = \boxed{a = 10}$$

$$Z_H = \frac{2400}{20.83} , \boxed{Z_H = 115.2 \Omega}$$

$$Z_L = \frac{240}{208.3} , \boxed{Z_L = 1.152 \Omega}$$

①  $I_{\phi_L} = \frac{5.41}{208.3} , \boxed{I_{\phi_L} = 26 \text{ mpu}} = 26 \times 10^{-3} \text{ per unit}$

$$I_{\phi_H} = \frac{5.41}{10} , \boxed{I_{\phi_H} = 26 \text{ mpu}} = 26 \times 10^{-3} \text{ per unit}$$

②  $Z_{eq(H)} = \frac{1.42 + 1.82j}{115.2} , \boxed{Z_{eq_H} = 0.0123 + 0.0158j}$   
↓ per unit

$$Z_{eq(L)} = \frac{0.0142 + 0.0182j}{1.152} , \boxed{Z_{eq_L} = 0.0123 + 0.0158j}$$
  
↓ per unit



Q5  $S = 10 \text{ KVA}$

Q

$$R_{eq} = \frac{P_{sc}}{I_{sc}^2} = \frac{120}{(22.2)^2}$$

$$R_{eq} = 0.243 \Omega \quad \text{--- (1)}$$

$$Z_{eq} = \frac{V_{sc}}{I_{sc}} = \frac{9.65}{22.2}$$

$$Z_{eq} = 0.4346 \Omega \quad \text{--- (2)}$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2} = \sqrt{(0.4346)^2 - (0.243)^2}, \quad X_{eq} = 0.36 \Omega$$


$$\cos \phi = \frac{P_{oc}}{V_{oc} I_{oc}} = \frac{80}{120 \times 4.2} = 0.159, \quad \theta = 80.85^\circ$$

$$R_c' = \frac{120}{4.2 \times 0.159}, \quad R_c' = 180 \Omega, \quad X_m' = \frac{120}{4.2 \times (\sin(80.85^\circ))}$$

$$X_m' = 29 \Omega, \quad a = \frac{450}{120} = 3.75$$

$$R_c = R_c' \times a^2 = 180 \times (3.75)^2 = 2531 \Omega$$
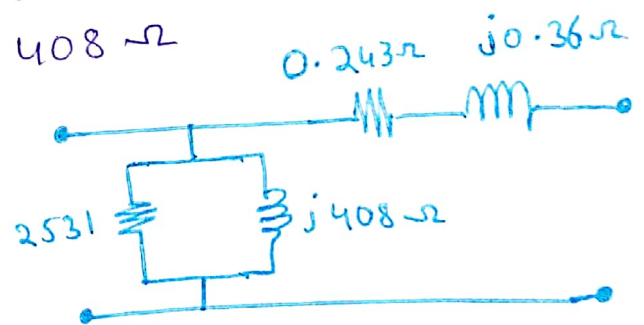
$$X_m = X_m' \times a^2 = 29 \times (3.75)^2 = 408 \Omega$$



$$I = \frac{10 \text{ K}}{120} = 83.3 \text{ A}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{120 \times 83.3 \times 0.8}{120 \times 83.3 \times 0.8 + 80 + 120} \times 100\%$$

$$\eta = 97.56\%$$

$$VR = \frac{450 + [(83.3 \angle -36.9^\circ)(0.243 + j0.36)] - 450}{R [(83.3 \angle -36.9^\circ)(0.243 + j0.36)]} \times 100\%$$

$$VR = 7.06\%$$

$$c) I = \frac{83.3}{2} = 41.67A$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100 \Rightarrow \frac{120 \times 41.67 \times 0.8}{120 \times 41.67 \times 0.8 + 80 + 30} \times 100$$

$$\boxed{\eta = 97.3 \%}$$

Q:-6

$$S = 150 \text{ MVA} , \quad 15-200 \text{ KV}$$


$$a) R = 1.2 \% , \quad X = 5 \% , \quad X_m = 80j \text{ pu}$$

$$Z_{base} = \frac{V_{base}}{I_{base}} = \frac{V_{base}}{\frac{P}{V_{base}}} = \frac{(V_{base})^2}{P} = \frac{15^2}{150} = 1.5$$

$$R = \left( \frac{1.2 \times 1.5}{100} \right) , \quad R = 0.018 \Omega$$

$$X = \left( \frac{5 \times 1.5}{100} \right) , \quad X = 0.075 \Omega , \quad X_m = (80 \times 1.5)$$

$$X_m = 120$$

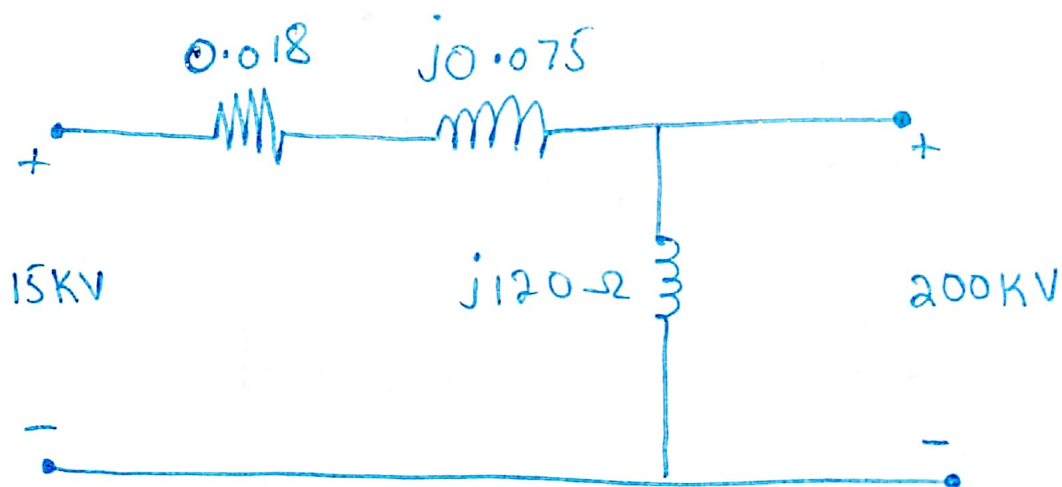

$$\textcircled{b} \quad I = \frac{150M}{15k} = 10kA = 10000 \angle -36.86^\circ$$

$$VR = \frac{R \left[ 15000 + (10000 \angle -36.86^\circ)(0.018 + j0.015) \right] - 15000}{R \left[ 15000 + (10000 \angle -36.86^\circ)(0.018 + j0.015) \right]} \times 100\%$$

$$VR = 3.85\%$$



$$\textcircled{c} \quad \text{Copper loss} = P_{\text{copper}} = (I^2)(R) = (10000)^2 \times (0.018)$$

$$P_{\text{copper}} = 1.8MW$$

Copper Core losses will be minimum let's say it will be zero because of no current flowing through the core (laminated core bars of transfo)

$\textcircled{d}$  0.8 lagging PF  $\rightarrow$

unity (1) PF  $\downarrow$

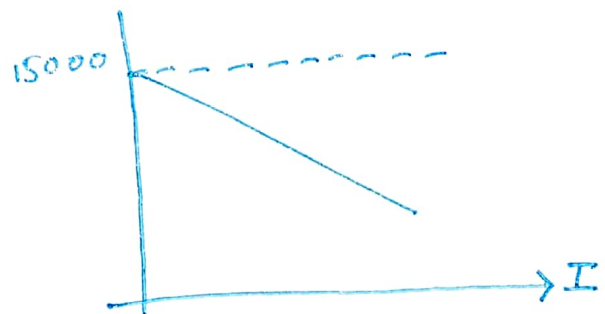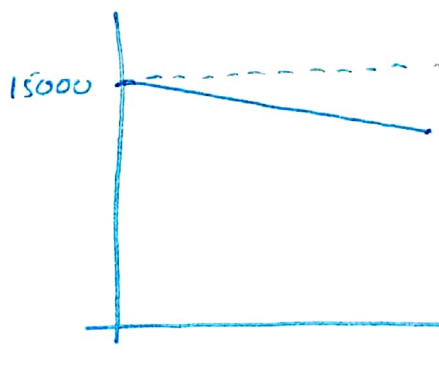

0.8 leading PF  $\downarrow$

