

Rafay Amir

Bsee19047

Machines Assignment 5

Q:1 $I_F = 5A$, $V_T = \sqrt{3} V_\phi$

① from the curve $E_L = 16.5 \text{ kV}$

$$E_\phi = \frac{16.5 \text{ kV}}{\sqrt{3}} = 9.526 \text{ kV}$$

load is delta connected with three impedance
 $24 \angle 25^\circ \Omega$

$$Z_\Delta = 24 \angle 25^\circ \Omega , Z_Y = \frac{Z_\Delta}{3} = 8 \angle 25^\circ \Rightarrow \text{singl phase}$$

$$V_\phi = I_A Z_Y \quad I_A = \frac{E_{\phi A}}{R_A + jX_s + Z} = \frac{9526}{0.2 + j2.5 + 8 \angle 25^\circ}$$


$$I_A = 1003.6 \angle -38.285^\circ \text{ A}$$

$$V_\phi = I_A Z_Y = (1003.6 \angle -38.29^\circ)(8 \angle 25^\circ) = 8029 \angle -13.3^\circ \text{ V}$$

$$V_T = (\sqrt{3})(V_\phi) = 13.9 \text{ kV}$$

② $E_A = V_\phi + Z_A I_A$
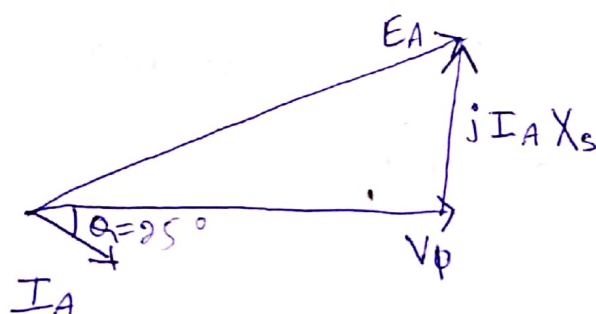
$$E_A = 8.03 \text{ kV} + (0.2 + j2.5)(1003.6 \angle -38.285^\circ) = 9.914 \angle 10.7^\circ \text{ kV}$$



$$\begin{aligned} \textcircled{c} P_{out} &= 3 V_{\phi} I_A \cos \theta \\ &= 3(8.029 \text{ kV})(1003.6) \cos(-13.3 + 38.28) \\ P_{out} &= 21.9 \text{ MW} \end{aligned}$$

$$P_{cu} = 3 I_A^2 R_A = 3(1003.6)^2(0.2) = 6040 \text{ kW}$$

$$\begin{aligned} P_{inp} &= P_{out} + P_{cut} + P_{cor} + P_{F+wo} \\ &= 21.9 \text{ MW} + 0.604 \text{ MW} + 1.5 \text{ MW} + 1 \text{ MW} \end{aligned}$$

$$P_{inp} = 25 \text{ MW}$$


$$\eta = \frac{P_{out}}{P_{inp}} \times 100 \Rightarrow 87.6 \%$$

d By adding another identical delta connected load ~~to~~ to the existing generator, the load current supplied by the generator increases due to this armature reactance drop increases which results in decrease in terminal voltage

$$\textcircled{e} Z_{\Delta} = 24 \angle 25^{\circ} \parallel 24 \angle 25^{\circ} = 12 \angle 25^{\circ}$$

$$Z_Y = \frac{Z_{\Delta}}{3} = 4 \angle 25^{\circ}$$
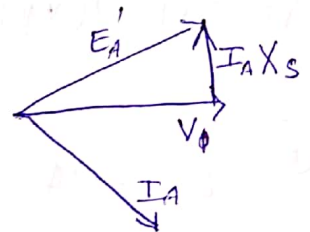
$$I_A = \frac{E_A}{R_A + jX_s + Z} = \frac{9526}{0.2 + j2.5 + 4 \angle 25^{\circ}} = 1679 \angle -47.6^{\circ} \text{ A}$$



$$V_{\phi} = I_A Z = 6715.7 \angle -22.6^{\circ} = 6716 \text{ V}$$

$$V_T = \sqrt{3} V_{\phi} = 11.632 \text{ kV}$$

(f) We can restore the terminal voltages by increasing the field current.

Q8-2

$$\textcircled{a} \quad n_m = \frac{120 f}{P} = \frac{(120)(50)}{20} = 300 \text{ rpm} = 31.4 \text{ rad/s}$$

$$\textcircled{b} \quad E_A = V_\phi + I_A Z$$

$$V_\phi = \frac{V_T}{\sqrt{3}} = 6928 \text{ V} = 1 \angle 0^\circ \text{ pu}$$

$$\therefore \theta = \cos^{-1}(0.85)$$

$$I = 1 \angle -31.78^\circ \text{ pu}$$

$$E_A = 1 \angle 0^\circ + (1 \angle -31.78^\circ)(0.1 + j0.9) = 1.714 \angle 24.55^\circ \text{ pu}$$

$$E_A = (1.714 \angle 24.55^\circ)(6928) = 11.87 \angle 24.55^\circ \text{ kV}$$

$$\textcircled{c} \quad \delta = 24.55^\circ$$

$$\textcircled{d} \quad Z_{\text{base}} = \frac{(V_{\phi \text{ base}})^2}{\frac{S_{\text{base}}}{3}} = \frac{(6928)^2}{\frac{200 \text{ M}}{3}} = 0.72 \Omega$$

$$R_A = (0.1)(0.72) = 0.072 \Omega$$

$$X_s = (0.9)(0.72) = 0.648 \Omega$$

$$\textcircled{e} \quad P_{\text{max}} = \frac{3 V_\phi E_A}{X_s} = \frac{3(6928)(11.875 \text{ kV})}{0.648} = 380 \text{ MW}$$

$$I_A = \frac{S}{\sqrt{3} V_L} = \frac{200 \text{ M}}{\sqrt{3} (12 \text{ kV})} = 9.622 \text{ kA}$$

$$P_{\text{out}} = 3 V_\phi I_A \cos \theta = 3(6928)(9.6225)(0.85)$$

$$P_{\text{out}} = 170 \text{ MW}$$

$$P = \frac{3V_{\phi} E_A}{X_s} \sin \theta$$

$$P = (380)(\sin(24.55^\circ))$$

$$P = 157.8 \text{ MW}$$

$$\text{Reverse power} = P_{\text{out}} - P = 170 \text{ M} - 157.8 \text{ M}$$

$$P_R = 12.2 \text{ MW}$$

$$\textcircled{f} \quad S^2 = P_{\text{out}}^2 + Q_{\text{max}}^2$$

$$Q_{\text{max}} = \sqrt{S^2 - P_{\text{out}}^2} = \sqrt{200^2 - (170^2)} = \sqrt{11100}$$

$$Q_{\text{max}} = 105.35 \text{ MVAR}$$

$$\textcircled{Q3} \quad 460 \text{ V}, \quad f = 60 \text{ Hz}$$

$$R_1 = 0.15, \quad X_m = 20 \Omega, \quad X_2 = 1.066 \Omega$$

$$R_2 = 0.154 \Omega, \quad X_1 = 0.852 \Omega, \quad P_{F+W} = 400 \text{ W}$$

$$P_{\text{misc}} = 150 \text{ W}, \quad P_{\text{core}} = 400 \text{ W}, \quad S = 0.02$$

$$\textcircled{a} \quad I_{\text{line}} = ?$$

$$Z_2 = R_2 + jX_2 + R_2 \left[\frac{1-S}{S} \right]$$

$$Z_2 = 0.154 + j1.066 + 0.154 \left[\frac{1-0.02}{0.02} \right] = j1.066 + 7.70$$

$$Z_F = Z_2 \parallel jX_m = \frac{jX_m Z_2}{Z_2 + jX_m} = \frac{(j20)(7.7 + j1.066)}{7.7 + j1.066 + j20}$$

$$Z_F = 6.32 \angle 28^\circ \Omega$$

$$I_L = I_A = \frac{V_{\phi}}{R_1 + jX_1 + Z_F} = \frac{266}{0.15 + j0.852 + 6.123 + j3.25}$$

$$I_L = I_A = 35.5 \angle -33^\circ \text{ A}$$

$$Z_T = R_1 + jX_1 + Z_T = 0.15 + j0.852 + 6.123 + j3.25$$

$$Z_T = 7.479 \angle 32.9^\circ$$

impedence angle is equals to 33°

③ $\phi = 32.9$

$$PF = \cos \phi = \cos (32.9) = 0.8396 \text{ lagging}$$

④ PF of rotor

$$PF = \cos \left[\tan^{-1} \frac{X_2}{R_2} \right] = \cos \left[\tan^{-1} \frac{1.066}{7.546} \right] = 0.9736 \text{ lagging}$$

$$f_r = s f_s$$

$$= (0.02)(60) = 1.2 \text{ Hz}$$

⑤ $P_{sc} = 3 I_A^2 R_1$

$$I_A = 35.5$$

$$P_{sc} = 3 (35.5)^2 (0.15) = 567 \text{ W}$$

⑥ $P_{AG} = P_{in} - P_{sc} - P_{core} =$

$$P_{AG} = 3 I_A^2 \frac{R_2}{s} = 3 (35.5)^2 (6.123) = 23.15 \text{ kW}$$

⑦ $P_{conv} = 3 I_A^2 R_2 \left(\frac{1-s}{s} \right) = \frac{3 I_A^2 R_2}{s} (1-s) = (23.15 \text{ kW})(1-0.07)$

$$P_{conv} = 22686 \text{ W}$$

⑧ $P_{in} = 3 V_\phi I_\phi \cos \phi = 3 (266) (35.5) \cos (0 + 32.9) = 23.785 \text{ kW}$

$$P_{out} = P_{conv} - P_{F+W} - P_{misc}$$

$$P_{out} = 22686 - 400 - 150 = 22136 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100 = \frac{22136}{23785} \times 100 = 93 \%$$

Q4 208V 60Hz

$$R_1 = 0.1 \Omega, R_2 = 0.07 \Omega$$

$$X_m = 10 \Omega, X_1 = 0.21 \Omega, X_2 = 0.21 \Omega$$

$$P_{\text{misc mech}} = 500W, P_{\text{misc}} = 0, P_{\text{core}} = 400W, s = 0.05$$

(a) $I_L = ?$

$$Z_2 = R_2 + jX_2 + R_2 \left(\frac{1-s}{s} \right) = 0.07 + j0.21 + 0.07 \left(\frac{1-0.05}{0.05} \right)$$

$$Z_2 = 1.415 \angle 8.536^\circ$$

$$Z_F = Z_2 \parallel X_m = (1.415 \angle 8.536^\circ) \parallel (j10) = 1.3185 + j0.3866$$

$$V_\phi = \frac{V_L}{\sqrt{3}} = \frac{208}{\sqrt{3}} = 120V$$

$$I_L = I_A = \frac{120}{0.1 + j0.21 + 1.3185 + j0.3866} = 77.98 \angle -22.81^\circ A$$

(b) $P_{\text{scL}} = 3I_A^2 R_1 = 3(77.98)^2(0.1) = 1824W$

(c) $P_{\text{AG}} = 3I_A^2 R_F = 3(77.98^2)(1.374) = 25000W$

(d) $P_{\text{conv}} = (1-s)P_{\text{AG}} = (1-0.05)(25000) = 23750W$

(e) $T_{\text{ind}} = \frac{P_{\text{AG}}}{W_{\text{sync}}} - \text{or} - W_{\text{sync}} = n_{\text{sync}} \times \frac{2\pi}{60}, n = \frac{120f}{P} = 1800 \text{ rpm}$

$$\omega = \frac{1800 \times 2\pi}{60} = 188.5$$

$$T = \frac{25000}{188.5} = 132.63 \text{ Nm}$$

$$\textcircled{f} \quad T_{\text{load}} = \frac{P_{\text{out}}}{\omega_m}$$

$$P_{\text{out}} = P_{\text{conv}} - P_{F+V} - P_{\text{misc}}$$

$$= 23750 - 500 - 0 = 23250 \text{ W}$$

$$n = (1 - 0.05)(1800) = 1710 \text{ rpm}$$

$$\omega = \frac{1710 \times 2\pi}{60} = 179.07 \text{ rad/s}$$

$$T = \frac{23250}{179.07} = 129.8 \text{ Nm} = T$$